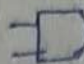
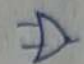
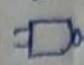


26-10-2023

INTERNAL STORAGE  $\rightarrow$  assembly (4 lines)  
 $\rightarrow$  hello. hex  
 ASSEMBLY

  $\rightarrow$  AND GATE  
  $\rightarrow$  OR GATE  
  $\rightarrow$  NAND GATE  
 LSR  $\rightarrow$  LOGICAL SHIFT RIGHT


GATE

PH2023, 24

/sd card / assembly # minim hello. asm

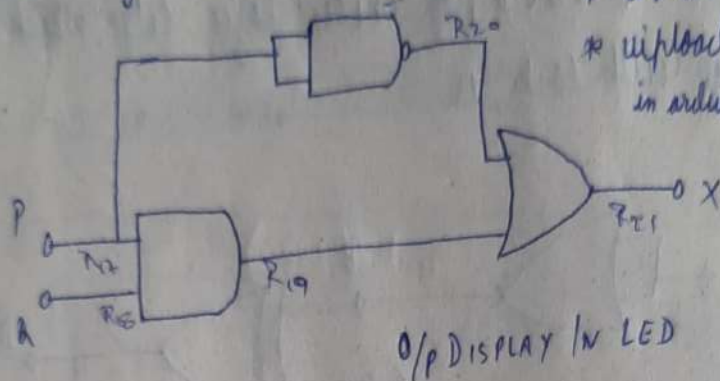Q 24. Which one of the following options is CORRECT for the given logic circuit?

\* minim. asm file  
 \* avrd. asm  
 \* upload precompiled in arduino board



O/P DISPLAY IN LED

SOLUTION:-

COMPLETED

- (A)  $P=1, A=1; X=0$
- (B)  $P=1, A=0; X=1$
- (C)  $P=0, A=0; X=0$
- (D)  $P=0, A=0; X=1$

SOLUTION:-

INPUTS  $\Rightarrow P, A$

OUTPUT  $\Rightarrow X$

P  $\Rightarrow$  BLUE  
 A  $\Rightarrow$  VIOLET

By Using binary algebra

TRUTH TABLE

X	P	A
0	0	0
0	0	1
1	1	0
1	1	1

$$X = \bar{P} + PA = \bar{P} + \bar{P}A = \bar{P} + A$$

$$P=0; A=0$$

$$X = \bar{P} + A$$

$$= \bar{0} + 0$$

$$= 1 + 0$$

$$X = 1$$

FILENAME = minim hello. asm  
 minim hello. asm

OPTION : D

.include "home/gadefat/  
 m328pdef.inc"

$$\therefore P=0; A=0; X=1$$

ARDUINO DROID  $\Rightarrow$  actions  $\rightarrow$  upload  $\rightarrow$  upload precompiled  $\rightarrow$  assembly  $\rightarrow$  hello. hex

31-10-2023

ASSEMBLY


COMPLETED

GATE

PM2023, 24

INTERNAL STORAGE  $\rightarrow$  assembly[41 items]  $\rightarrow$  hello. hex

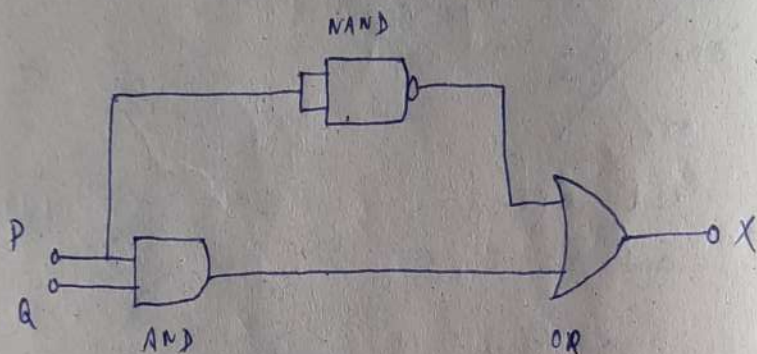Q24. Which one of the following options is correct for the given logic circuit?



SOLUTION:-

By using binary algebra

$$X = \bar{P} + PA = \bar{P} + \bar{P}A = \bar{P} + A$$

$$P = 0; A = 0$$

$$X = \bar{P} + A$$

$$= \bar{0} + 0$$

$$= 1 + 0$$

$$X = 1$$

Op:- Display On LED

$$\therefore P = 0; A = 0; X = 1$$

TRUTH TABLE:-

P	Q	X
0	0	1
0	1	1
1	0	0
1	1	1



CODE :-

```
-> .include "/sdcard/digital-design/assembly/setup/m328Pdef/m328Pdef.inc" ; Include file for ATmega328P

-> ldi r16, 0b11111001

-> out DDRB, r16

-> Start:

-> in r17, PINB

-> in r18, PINB

-> lsl r17

-> lsl r17

-> lsl r18

-> and r17, r18

-> lsl r18

-> lsl r18

-> and r18, r18

-> com r18

-> lsl r17

-> lsl r17

-> lsl r18

-> or r17, r18

-> out PORTB, r17

-> rjmp start
```

[P.T.O.]

STORAGE PATH  
FILES  $\Rightarrow$

INTERNAL STORAGE  $\rightarrow$  assembly[4 ITEMS]  $\rightarrow$  hello.hex

TERMX:-

/sdcard / assembly # mvim hello.asm

FILE NAME:-

mvim hello.asm

INPUTS  $\Rightarrow$  P ; Q

$\left\{ \begin{array}{l} P \rightarrow \text{BLUE JUMPER WIRE} \\ Q \rightarrow \text{VIOLET JUMPER WIRE} \end{array} \right\}$

OUTPUT  $\Rightarrow$  X

1  $\rightarrow$  LED "ON"

TRUTH TABLE:-

P	Q	X
0	0	1
0	1	1
1	0	0
1	1	1

\* mvim.asm file


\* arduino.asm { arduino.asm }

\* upload precompiled in arduino board

CONNECTIONS  $\Rightarrow$  ARDUINO TO BREAD BOARD

ARDUINO	BREAD BOARD
GROUND	GROUND
5V	+ve
PIN-9	+ve [5V]
PIN-10	-ve
PIN-13	LED

LED  $\Rightarrow$



~~LED~~ LED

+ve


-ve

BREAD BOARD


ANYWHERE CONNECTED TO 13 PIN OF ARDUINO

GROUND




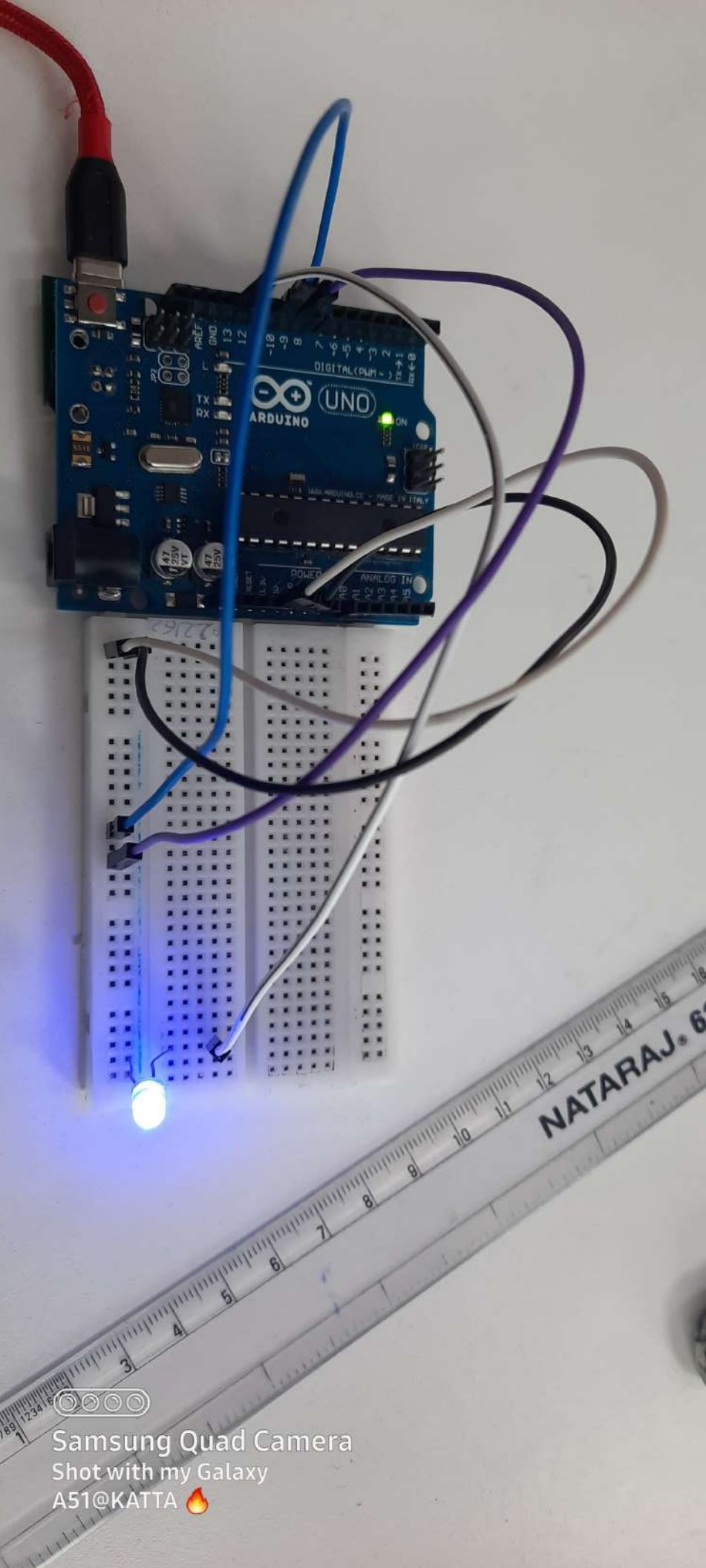


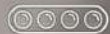Samsung Quad Camera  
Shot with my Galaxy  
A51@KATTA 🔥



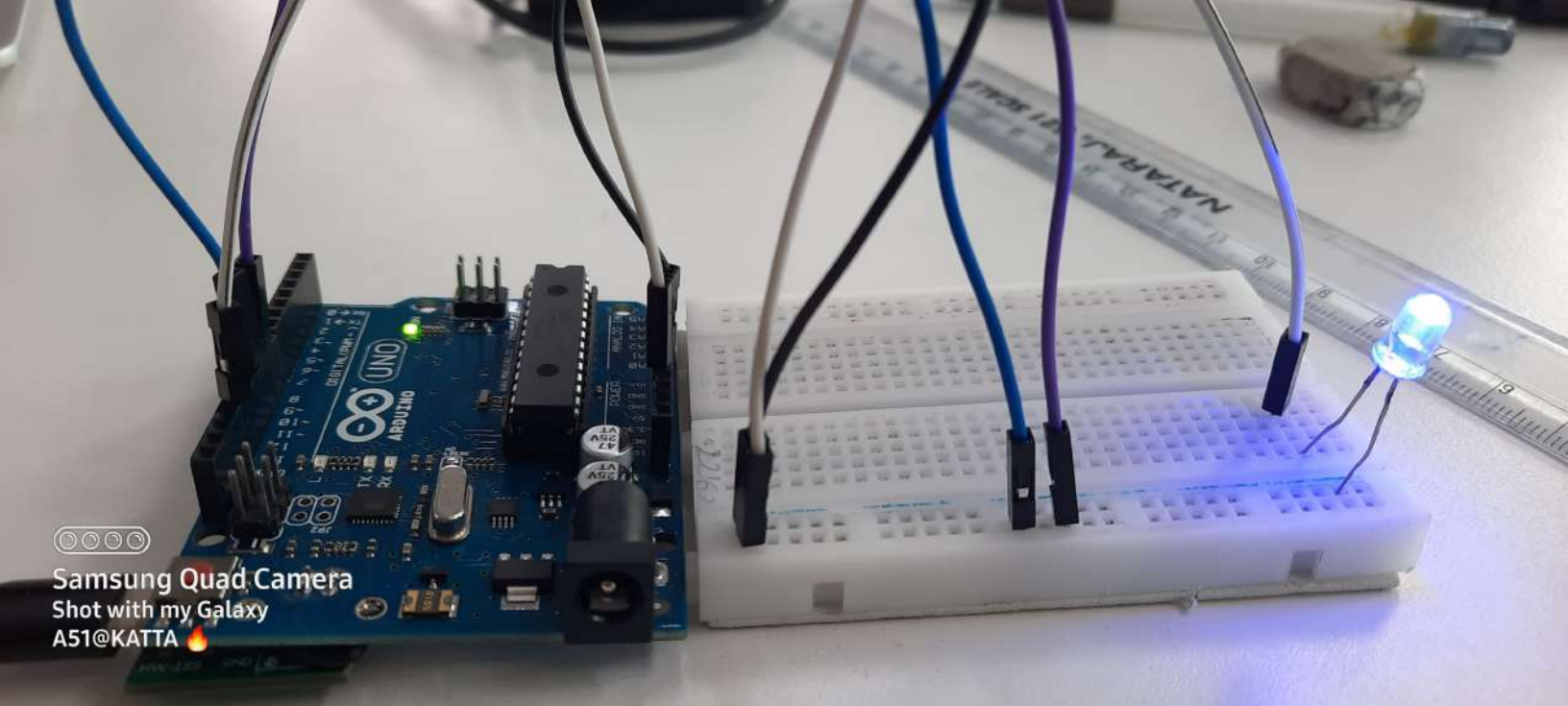
Samsung Quad Camera  
Shot with my Galaxy  
A51@KATTA 🔥



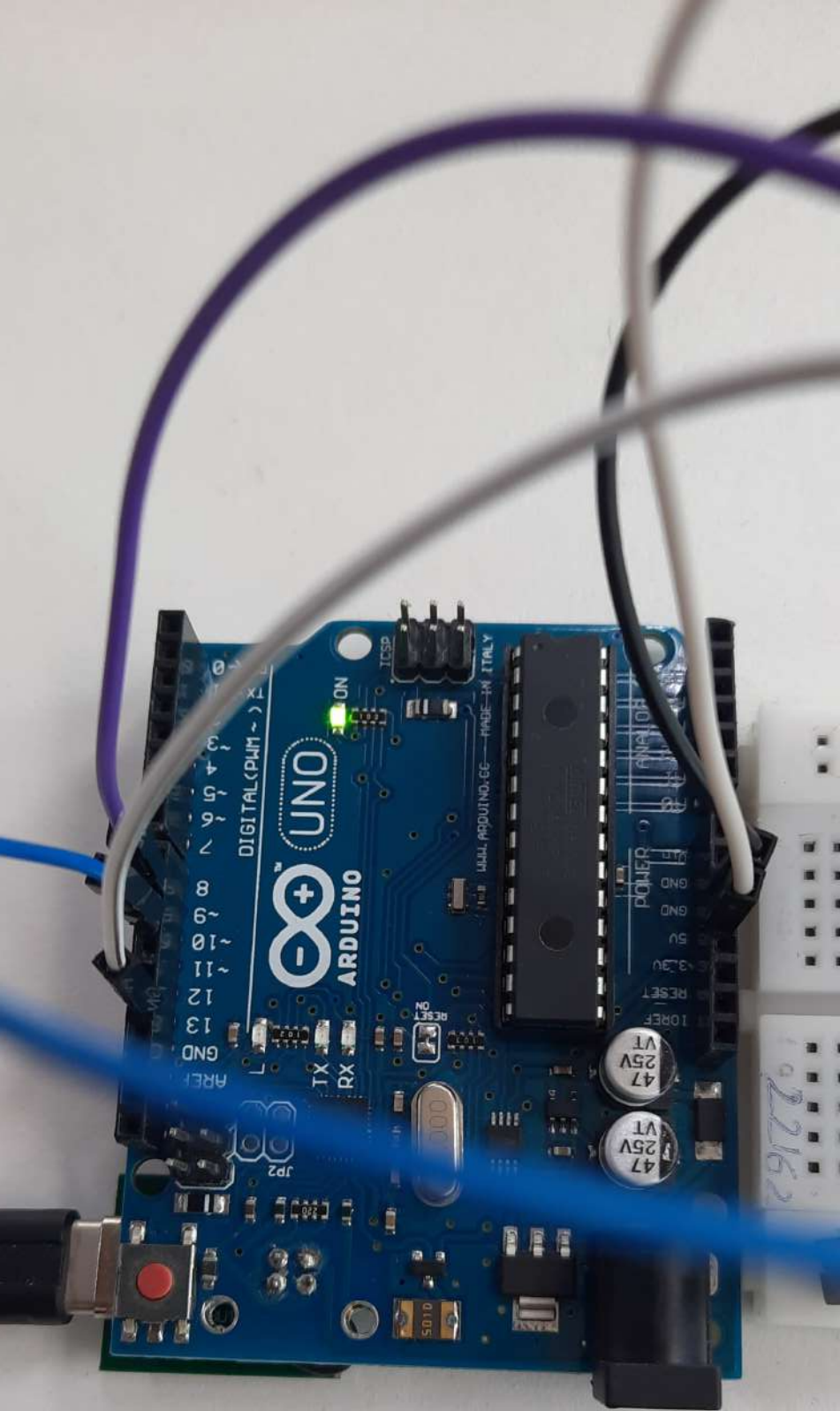

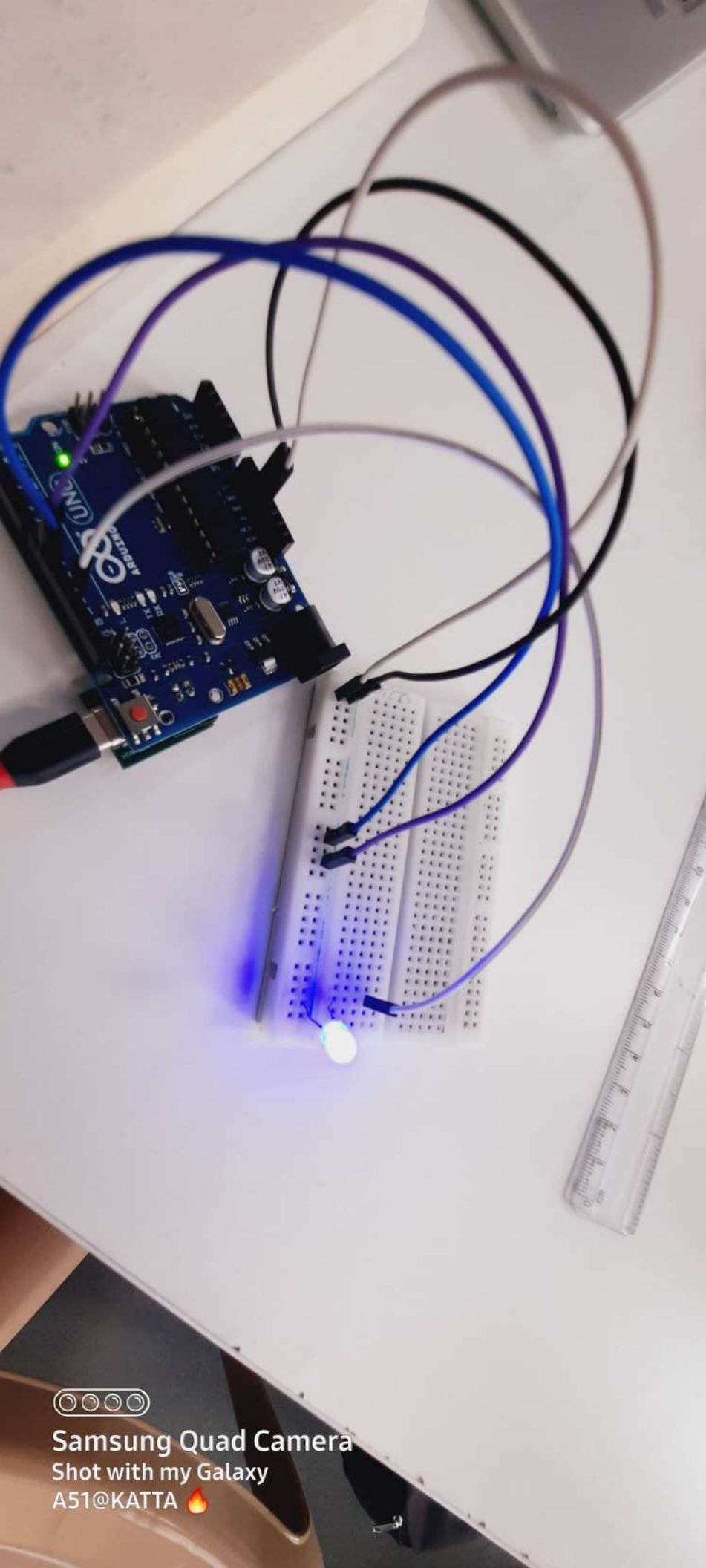
Samsung Quad Camera  
Shot with my Galaxy  
A51@KATTA 🔥





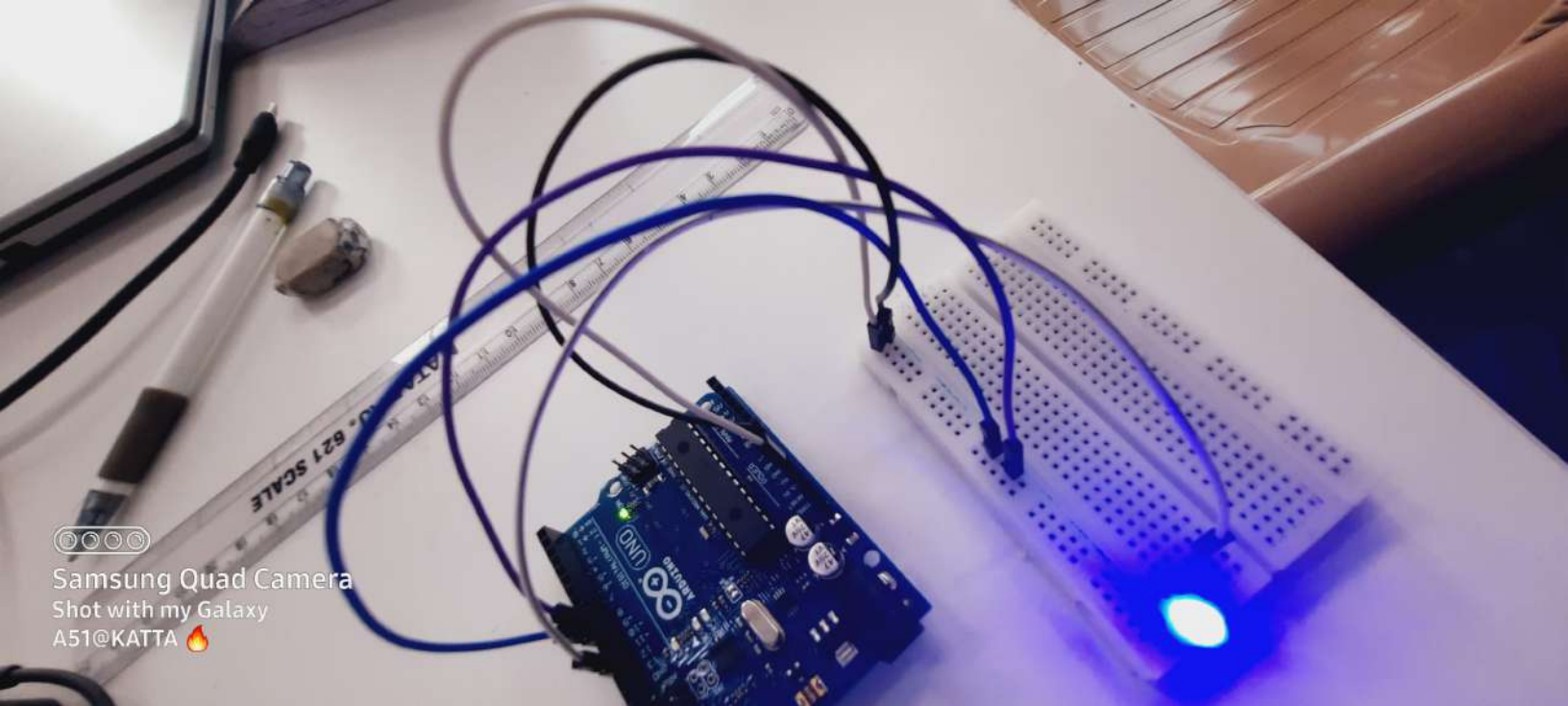Samsung Quad Camera  
Shot with my Galaxy  
A51@KATTA 🔥






Samsung Quad Camera

Shot with my Galaxy

A51@KATTA 🔥

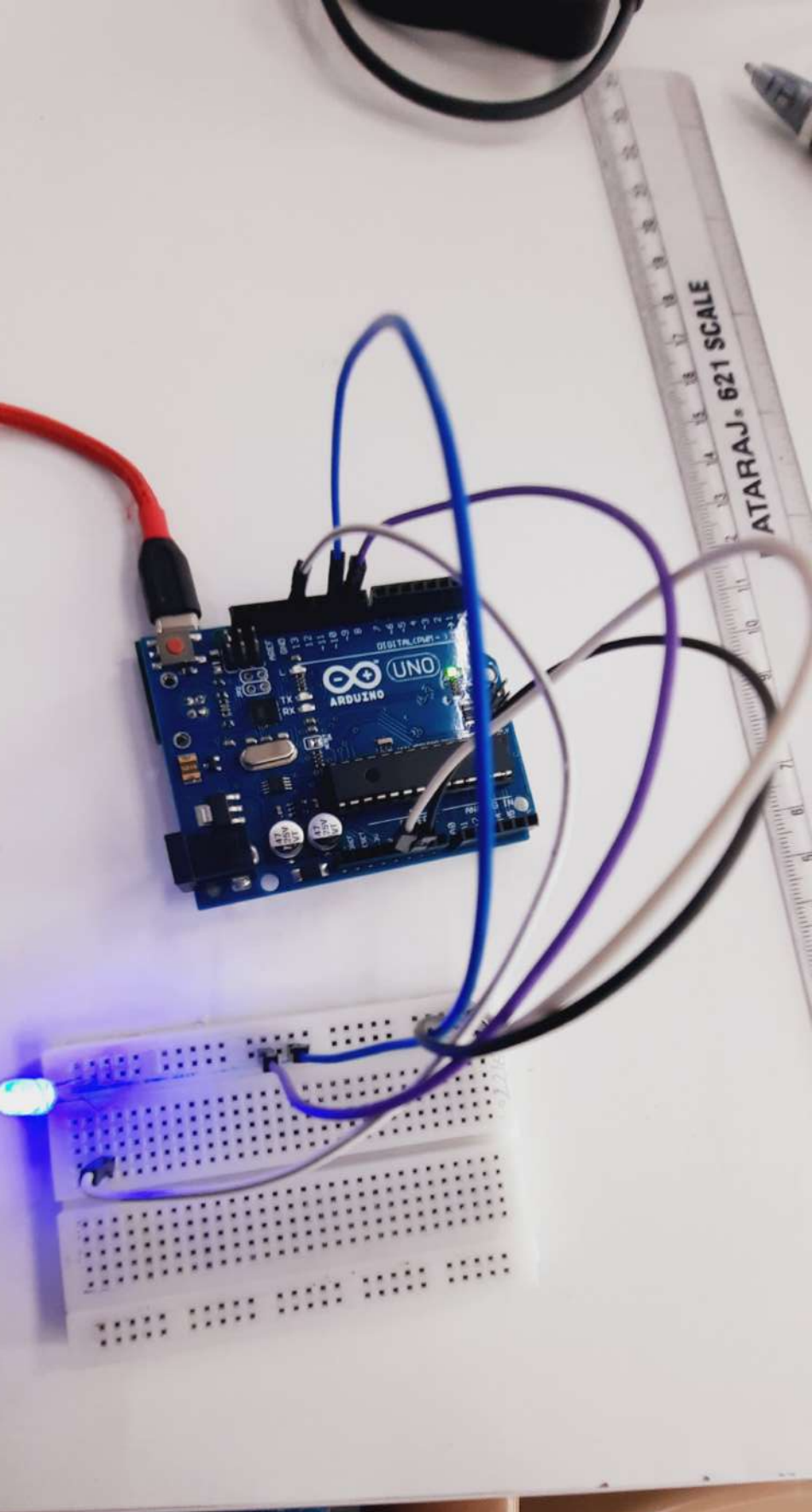

Samsung Quad Camera  
Shot with my Galaxy  
A51@KATTA 🔥