
## GATE EC 2023

## Hemant

## October 2023

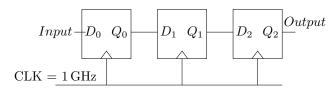1. The synchronous sequential circuit shown below works at a clock frequency of 1 GHz. The throughput, in Mbit  $\rm s^{-1}$  and the latency, in ns, respectively, are



- (a) 1000, 3
- (b) 333.33,1
- (c) 2000, 3
- (d) 333.33,3

(GATE EC 2023)